
(DEEMED TO BE UNIVERSITY)

Gram: Rupa-Ki-Nangal, Post: Sumel, Via: Jamdoli, Jaipur-302031, Rajasthan, India

Microwave Engineering Theory
2nd Year ECE Project

Date of Submission: 29/04/23

NAME: SIDDHANT JAIN

ROLL NO: 22UEC132

Name of Project 1 (Part-A):

I. Question 7:

Design a stepped-impedance low-pass filter having a cutoff frequency of 3 GHz, and a fifth-order 0.5 dB equal-ripple response. Assume $R_0=50\Omega$, $Z_{i1}=15\Omega$, and $Z_{i2}=120\Omega$.


- Find the required electrical lengths of the five sections
- Use Ansoft Designer to plot the insertion loss from 0 to 6 GHz.
- Lay out the microstrip implementation of the filter on an FR4 substrate having $\epsilon_r = 4.2$, $d = 0.079$ cm, $\tan\delta = 0.02$, with copper conductors 0.5 mil thick. Use ADS to plot the insertion loss versus frequency in the passband of the filter.

II. Simulation Platform:

ANSOFT DESIGNER SOFTWARE

III. Design and Analysis:

(a) Screenshots of schematics

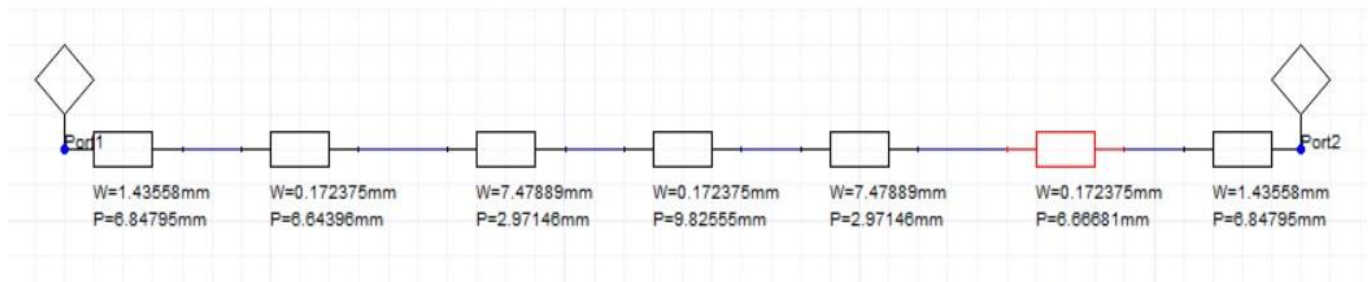

(b) calculations

Siddhant Jain 22VE132

Microwave Engineering

Assignment

Part A [Question 7]

$$f_c = 3 \text{ GHz}$$

$$N = 5$$

$T_{\text{gro}} = 0.5 \text{ dB}$, Equal ripple response

$$R_0 = 50 \Omega$$

$$Z_0 = 15 \Omega$$

$$Z_n = 120 \Omega$$

Electrical length $= \beta l = \frac{Z_0 l}{Z_n}$ for inductor $\beta l = \frac{Z_0 l}{Z_0}$ for capacitor

Prototype Elements

$$g_0 = 1$$

$$g_1 = \frac{a_1}{F_2}$$

$$g_k = \frac{a_{k-1} a_k}{b_{k-1} g_{k-1}}$$

$$g_{n+1} = \begin{cases} 1 & \text{for } n \text{ odd} \\ \coth^2(F_1) & \text{for } n \text{ even} \end{cases}$$

where $F_1 = \frac{1}{4} \ln \left\{ \coth h \left(\frac{L_n}{17.372} \right) \right\}$

$$F_2 = \sinh \left(\frac{2F_1}{N} \right)$$

$$a_k = 2 \sin \left\{ \frac{(2k-1)\pi}{2n} \right\} \quad k = 1, 2, \dots, n$$

$$b_k = F_2^2 + \sin^2 \left(\frac{k\pi}{n} \right) \quad k = 1, 2, \dots, n$$

$$F_1 = \frac{1}{4} \ln \left\{ \coth h \left(\frac{L_n = 0.5}{17.372} \right) \right\} = 0.887$$

$$F_2 = \sinh \left(\frac{2 \times 0.887}{5} \right) = 0.362$$

$$a_1 = 2 \sin \frac{\pi}{10} = 0.617$$

$$a_3 = 2 \sin \left(\frac{3\pi}{10} \right) = 1.44$$

$$a_2 = 2 \sin \left(\frac{3\pi}{10} \right) = 1.617$$

$$a_n = 2 \sin \left(\frac{7\pi}{10} \right) = 1.614$$

Richard Jon
 22UEC132

$$a_5 = 2 \sin\left(\frac{4\pi}{10}\right) = 0.62$$

$$b_1 = (0.362)^2 + \sin^2\left(\frac{\pi}{5}\right) = 0.131 + 0.345 \Rightarrow 0.476$$

$$b_2 = (0.362)^2 + \sin^2\left(\frac{2\pi}{5}\right) = 0.131 + 0.904 = 1.035$$

$$b_3 = (0.362)^2 + \sin^2\left(\frac{3\pi}{5}\right) = 0.131 + 0.905 = 1.036$$

$$b_4 = (0.362)^2 + \sin^2\left(\frac{4\pi}{5}\right) = 0.131 + 0.346 = 0.477$$

$$b_5 = (0.362)^2 + \sin^2\left(\frac{5\pi}{5}\right) = 0.131 + 0 = 0.131$$

$$g_1 = \frac{a_1}{F_2} = \frac{0.617}{0.362} = 1.704 \qquad g_2 = \frac{a_1 a_2}{b_1 a_1} \Rightarrow \frac{0.617 \times 1.617}{0.476 \times 1.704} \Rightarrow 1.23$$

$$g_3 = \frac{a_2 a_3}{b_2 g_2} \Rightarrow \frac{1.617 \times 1.44}{1.035 \times 1.23} = 2.52 \qquad g_4 = \frac{a_3 a_4}{b_3 g_3} \Rightarrow \frac{1.44 \times 1.619}{1.036 \times 2.52} \Rightarrow 1.23$$

$$a_5 = \frac{a_4 a_5}{b_4 g_4} \Rightarrow \frac{1.619 \times 0.62}{0.477 \times 1.23} \Rightarrow 1.71$$

$$\textcircled{1} \beta_l = \frac{20L}{2n} \Rightarrow \frac{50 \times 1.704}{120} \Rightarrow 40.70^\circ$$


$$\textcircled{2} \beta_l = \frac{24L_2}{2n} \Rightarrow \frac{15 \times 1.23}{60} = 0.309 \Rightarrow 21.15^\circ$$

$$\textcircled{3} \beta_l = \frac{20L_3}{2n} \Rightarrow \frac{50 \times 2.52}{120} \Rightarrow 1.05 \Rightarrow 60.14^\circ$$


$$\textcircled{4} \beta_l = \frac{24L_4}{2n} \Rightarrow \frac{15 \times 1.23}{50} \Rightarrow 0.369 \Rightarrow 21.15^\circ$$

$$\textcircled{5} \beta_l = \frac{20L_5}{2n} \Rightarrow \frac{50 \times 1.71}{120} \Rightarrow 0.7125 \Rightarrow 40.84^\circ$$

(c) 3D Layout

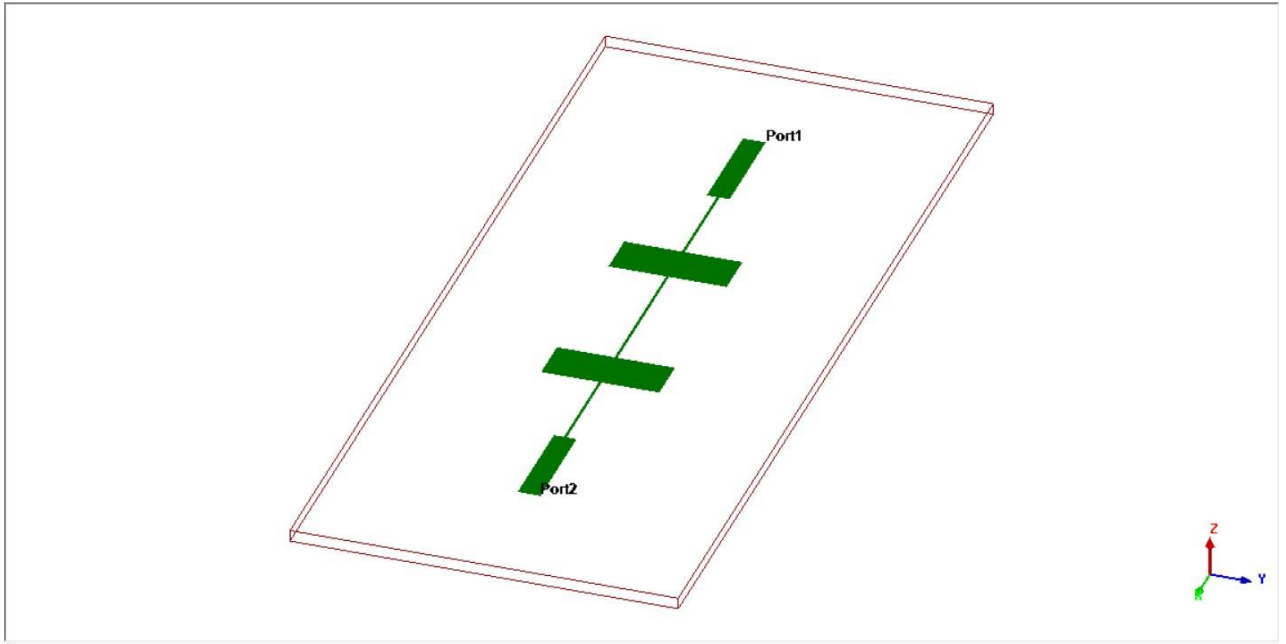

(d) Analysis of the results.

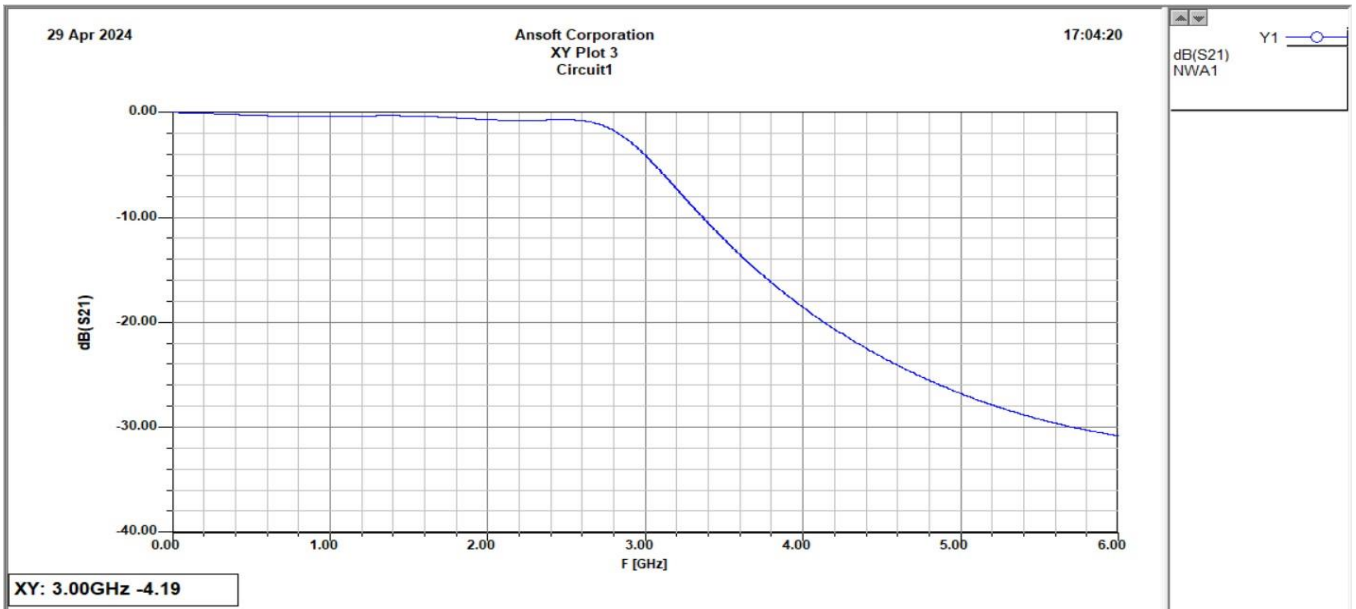

IV. Conclusion

We successfully implemented 0.5db equal ripple filter with cutoff frequency of 3GHz.

Name of Project 2 (Part-B):

I. Question 11:

Design a Wilkinson power divider with a power division ratio of $P_3/P_2=1/5$, and a source impedance of 50Ω .

- Show all calculations
- Design the schematic diagram.
- Use Ansoft Designer to plot the S_{12} , S_{21} , S_{32} versus frequency.

II. Simulation Platform:



ANSOFT DESIGNER SOFTWARE

III. Design and Analysis:

(a) Screenshots of all schematics

Siddhant Jain
22 DEC 132

Schematic

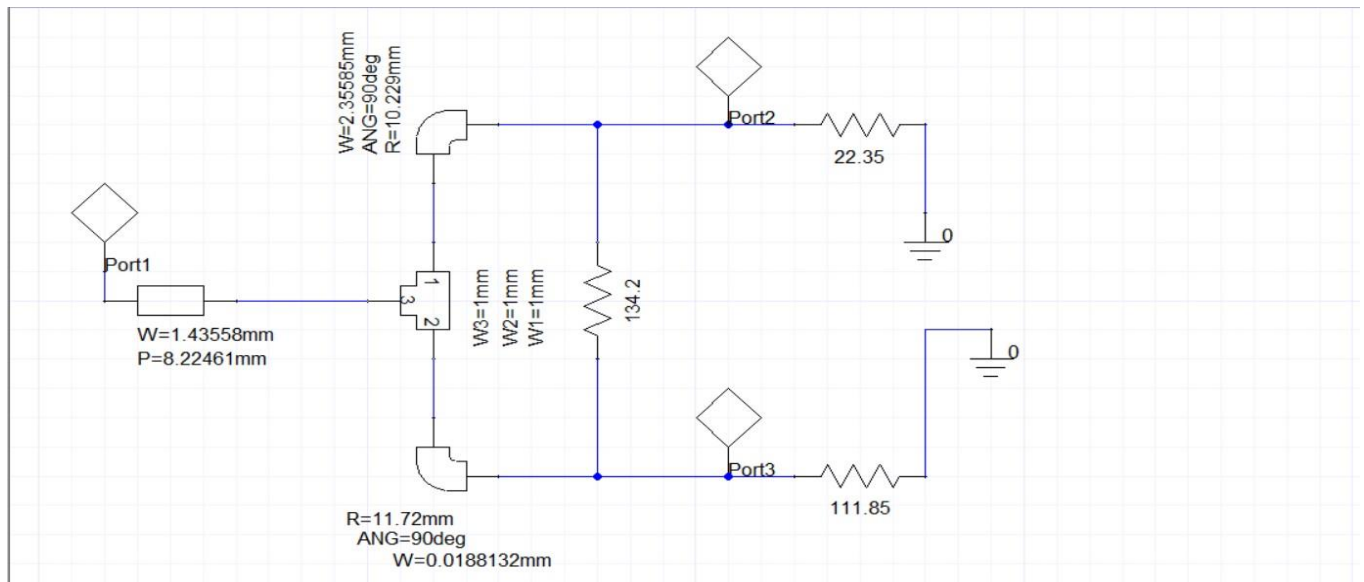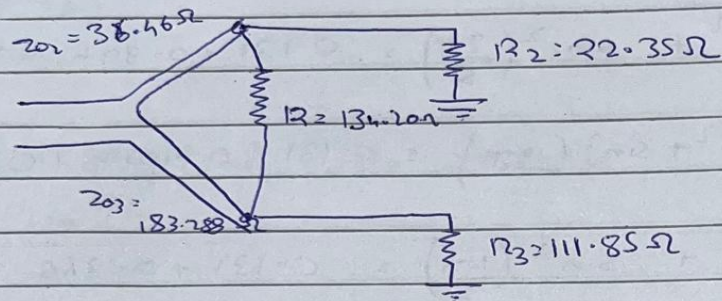

(b) Screenshots of results.

1

Part B [Question 11]

$$\frac{P_3}{P_2} = \frac{1}{5} \quad k^2 = \frac{1}{5}, \quad k = \frac{1}{\sqrt{5}} = 0.447 \quad Z_0 = 50 \Omega$$

$$Z_{02} = Z_0 \sqrt{k(1+k^2)} \Rightarrow 50 \sqrt{0.447(1.44)} \Rightarrow \boxed{36.46 \Omega}$$

$$Z_{03} = Z_0 \sqrt{\frac{1+k^2}{k^3}} \Rightarrow 50 \sqrt{\frac{1+(0.447)^2}{(0.447)^3}} \Rightarrow 50 \sqrt{\frac{1+0.199}{0.0893}} \Rightarrow 50 \sqrt{13.43}$$


$$\boxed{Z_{03} = 183.288 \Omega}$$

$$R = Z_0 \left(k + \frac{1}{k} \right) \Rightarrow 50 \left[0.447 + \frac{1}{0.447} \right] \Rightarrow \boxed{134.30 \Omega}$$


$$R_2 = Z_0 k = 50 \times 0.447 \Rightarrow \boxed{22.35 \Omega}$$

$$R_3 = \frac{Z_0}{k} \Rightarrow \frac{50}{0.447} \Rightarrow \boxed{111.85 \Omega}$$

(c) Layout with dimensions

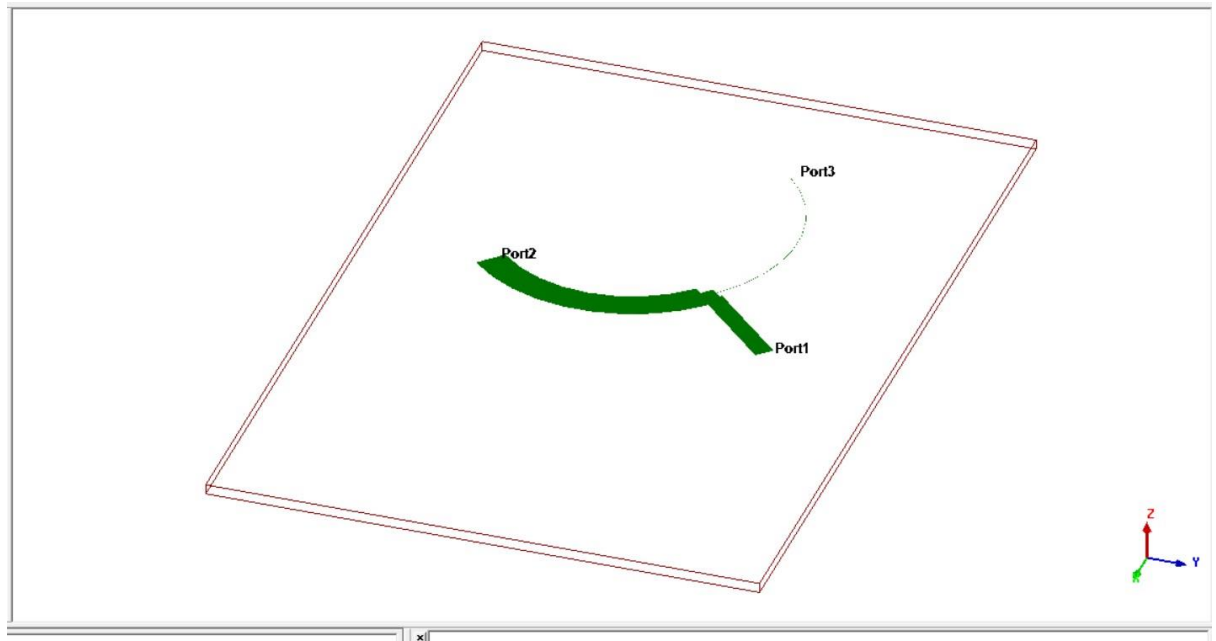

(d) Analysis of the results.

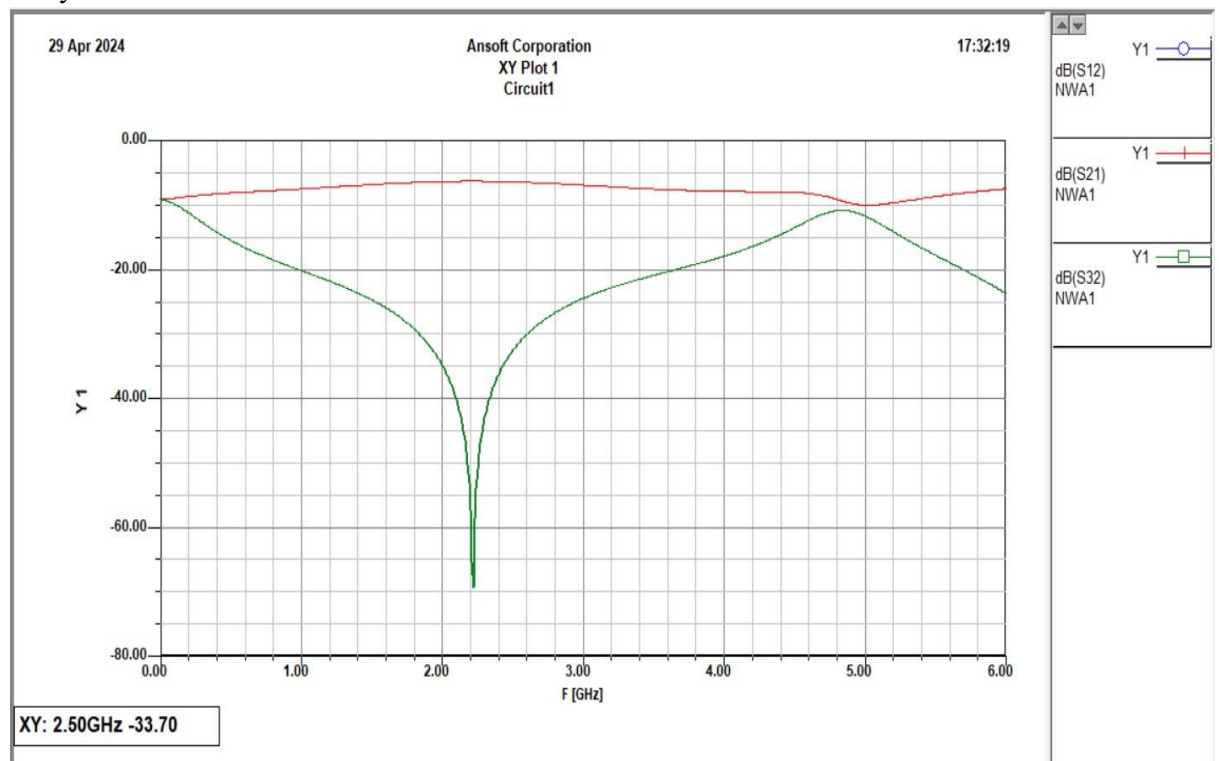

IV. Conclusion

We successfully made a Wilkinson unequal power divider with $P3/P2 = 1/5$ and cutoff frequency = 2.5GHz.

Question 12:

I. Question

Design a branch line coupler with equal power division ratio at 2 GHz.



- Show all calculations
- Design the schematic diagram.
- Design the layout on FR4 substrate (4.4) with thickness of 0.8mm.
- Use Ansoft Designer to plot the S_{11} , S_{21} , S_{31} , S_{41} , versus frequency.

II. Simulation Platform

ANSOFT DESIGNER SOFTWARE

III. Design and Analysis:

a) Screenshots of all schematics

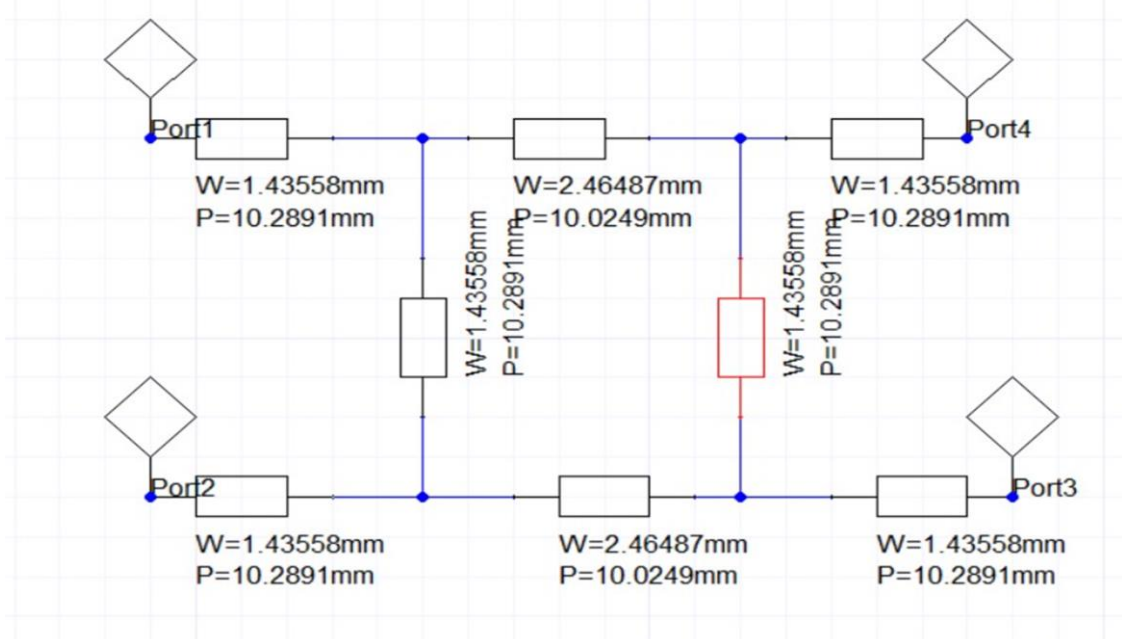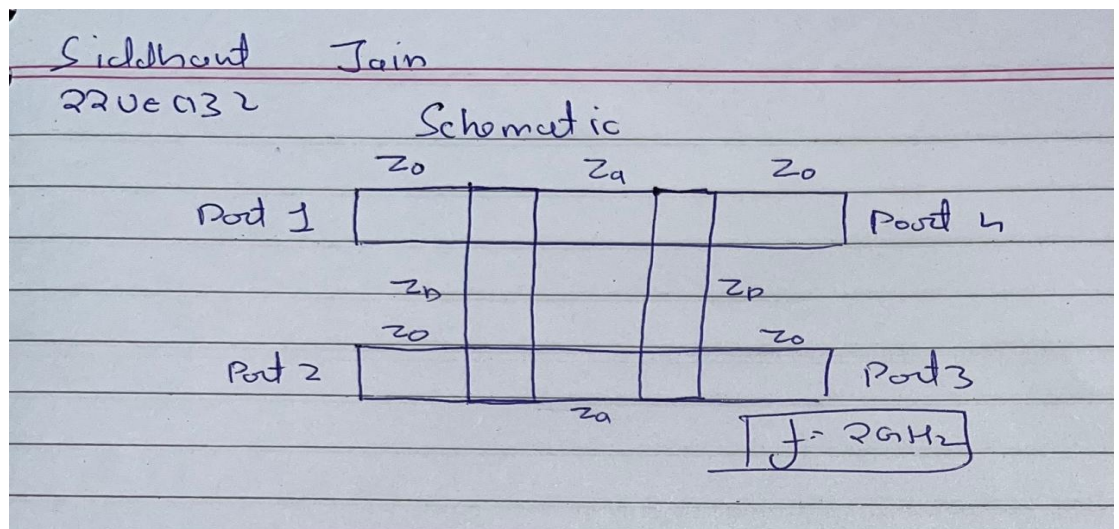

b) Screenshots of Results


[Question 12]

Branch line coupler with equal power division


$$Z_0 = 50 \Omega$$
$$Z_b = Z_0 = 50 \Omega$$
$$Z_g = \frac{Z_0}{\sqrt{2}} = \frac{50}{\sqrt{2}} \Rightarrow 35.35 \Omega$$

$f_c = 2 \text{ GHz}$

c) Layout with dimensions

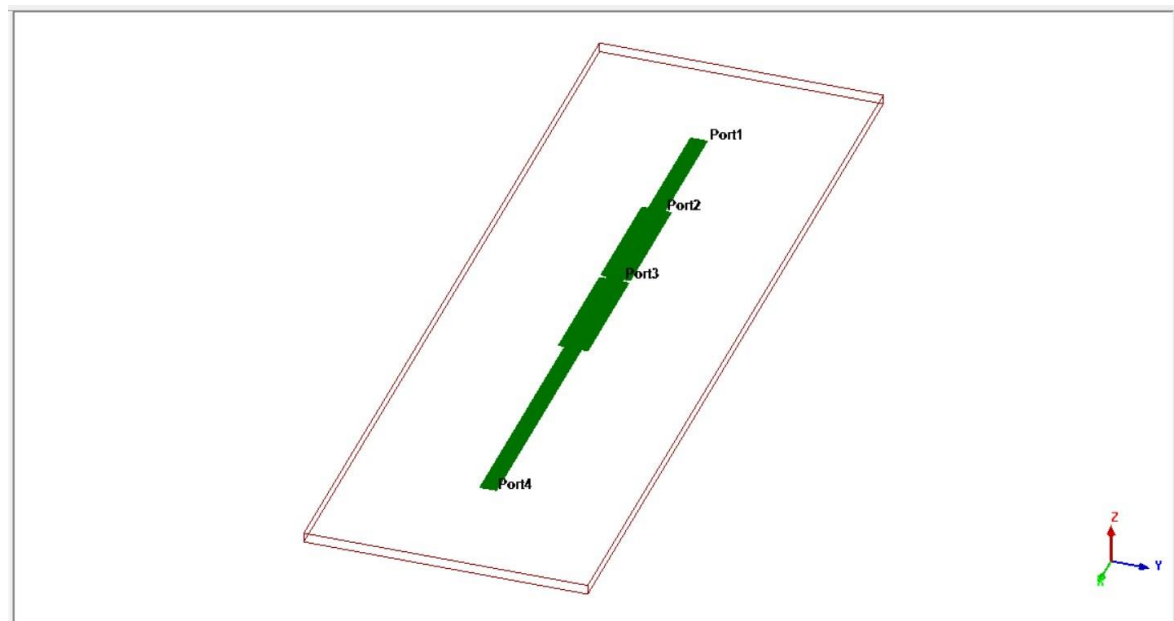

d) Analysis of the results.

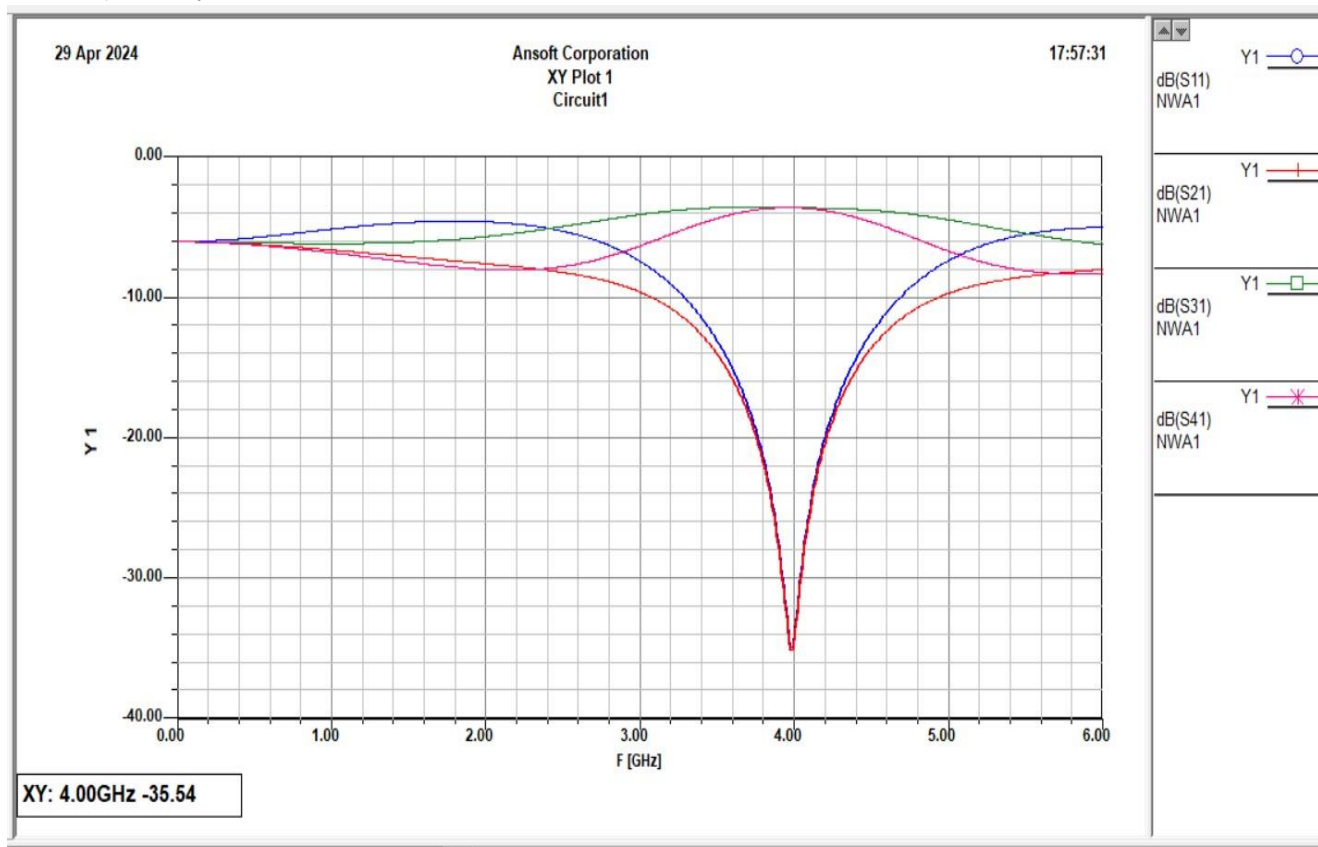

IV. Conclusion

We successfully made a Branch line Coupler with Equal power division at 2 GHz with line impedance equal to 50 ohm.
